

Question: Implement a 4 bit ALU that takes two 4 bit numbers A(A3,A2,A1,A0) and B(B3,B2,B1,B0) and has S2, S1 & S0 as three selection switches to implement the given truth table.

S2	S1	S0	Output	Function
0	0	0	Ai	Buffer A
0	0	1	Ai'	NOT A
0	1	0	Bi	Buffer B
0	1	1	Bi'	NOT B
1	0	0	Ai AND Bi	AND
1	0	1	Ai OR Bi	OR
1	1	0	Ai XOR Bi	XOR

Design Instructions:

- Core Unit: Build a 4-bit ALU by cascading four 1-bit Full Adder slices.
- The Rule: You cannot use a ready-made MUX for input selection.
- The Steps:
 1. Find what Xi and Yi must be for each selection line S2, S1, S0 combination.
 2. Use K-Maps to find the simplest Boolean equations for Xi and Yi and Cin.
 3. Build this selection logic using basic gates and connect it to the Full Adder.

Table-1: Condensed Function Table of the ALU Logic Unit

S0	S1	S2	Xi	Yi	Zi	Output
0	0	0	Ai	0	0	Ai
0	0	1	Ai	1	0	Ai'
0	1	0	0	Bi	0	Bi
0	1	1	1	Bi	0	Bi'
1	0	0	Ai.Bi	0	0	Ai AND Bi
1	0	1	Ai+Bi	0	0	Ai OR Bi
1	1	0	Ai	Bi	0	Ai XOR Bi

Explanation:

1.When Selection line- S0 S1 S2 = 000

Here the output is Ai, so A is passed directly. That's why Xi = Ai is selected. Since no modification is needed, Yi = 0 and Zi = 0. This combination simply keeps A unchanged, so the output becomes Ai (Buffer A).

2.When Selection line- S0 S1 S2 = 001

Here the output is Ai', meaning A must be inverted. So we still keep Xi = Ai, but now we need inversion, so Yi = 1. Zi = 0 because no extra operation is required. This produces NOT A.

3.When Selection line- $S_0 S_1 S_2 = 010$

Here the output is B_i , so B is passed directly. That's why $Y_i = B_i$ is chosen as the main input, while $X_i = 0$ (A is not used). $Z_i = 0$ since no operation is needed. This gives Buffer B.

4.When Selection line- $S_0 S_1 S_2 = 011$

Here the output is B_i' , so B must be inverted. We keep $Y_i = B_i$, but now inversion is needed, so $X_i = 1$ is used to flip it. $Z_i = 0$. This produces NOT B.

5.When Selection line- $S_0 S_1 S_2 = 100$

Here the output is $A_i \text{ AND } B_i$. So both inputs are needed together. That's why $X_i = A_i \cdot B_i$ (AND combination is prepared directly), while $Y_i = 0$ and $Z_i = 0$. This gives the AND result.

6.When Selection line- $S_0 S_1 S_2 = 101$

Here the output is $A_i \text{ OR } B_i$. Again both inputs are needed, but now in OR form. So $X_i = A_i + B_i$ is selected, $Y_i = 0$, and $Z_i = 0$. This produces the OR output.

7.When Selection line- $S_0 S_1 S_2 = 110$

Here the output is $A_i \text{ XOR } B_i$. So both inputs are used separately: $X_i = A_i$ and $Y_i = B_i$. With $Z_i = 0$, the circuit produces XOR behavior. This gives the final XOR result.

Table-2: Truth Table of the ALU Logic Unit

S0	S1	S2	Bi	Ai	Xi	Yi	Zi	Output
0	0	0	0	0	0	0	0	BUFFER (Ai)
				1	1			
			1	0	0	0		
				1	1			
0	0	1	0	0	0	1	0	NOT (Ai)
				1	1			
			1	0	0	1		
				1	1			
0	1	0	0	0	0	0	0	BUFFER (Bi)
				1	0			
			1	0	0	1		
				1	0			
0	1	1	0	0	1	0	0	NOT (Bi)
				1	1			
			1	0	1	1		
				1	1			
1	0	0	0	0	0	0	0	AND (Ai AND Bi)
				1	0			
			1	0	0	0		
				1	1			
1	0	1	0	0	0	0	0	OR (Ai OR Bi)
				1	1			
			1	0	1	0		
				1	1			
1	1	0	0	0	0	0	0	XOR (Ai XOR Bi)
				1	1			
			1	0	0	1		
				1	1			

K-Map

1.K-map For Xi:

A=0

DE \ BC	00	01	11	10
00	0 0	0 1	1 3	1 2
01	0 4	0 5	1 7	1 6
11	1 12	1 13	1 15	1 14
10	0 8	0 9	0 11	0 10

A=1

DE \ BC	00	01	11	10
00	0 16	0 17	1 19	0 18
01	0 20	1 21	1 23	1 22
11	0 28	0 29	0 31	0 30
10	0 24	0 25	1 27	1 26

Simplified Boolean Expression

$$A'B'D + A'BC + AB'CE + ABC'D + B'CD$$

Let, $A=S_0$, $B=S_1$, $C=S_2$, $D=A_i$, $E=B_i$

So,

The Final simplified boolean expression is:

$$X = S_0'S_1'A_i + S_0'S_1S_2 + S_0S_1'S_2B_i + S_0S_1S_2'A_i + S_1'S_2A_i$$

2.K-Map For Yi:

$\begin{array}{c} CD \\ AB \end{array}$		00	01	11	10
00		0 0	0 1	1 3	1 2
01		0 4	1 5	1 7	0 6
11		0 12	1 13	0 15	0 14
10		0 8	0 9	0 11	0 10

Simplified Boolean Expression

$$A'B'C + A'CD + BC'D$$

Again


Let, $A=S_0$, $B=S_1$, $C=S_2$, $D=A_i$, $E=B_i$

So,

The Final simplified boolean expression is:


$$Y = S_0'S_1'S_2 + S_0'S_2A_i + S_1S_2'A_i$$

ALU-Circuit

 

There is no gate for Zi here because we always get Zi=0. And don't get Zi=1.

1-bit ALU

 

Logisim circuit attached in another file.